

# Hardware Assignment Report

## Random Number Generation using Shift Registers

CS22BTECH11046

P.Yasaswini

### COMPONENTS.

Components	Value	Quantity
Breadboard		1
Seven Segment Display	Common Anode	1
Decoder	7447	1
Flip Flop	7474	2
X-OR GATE	7486	1
555 IC		1
Resistor	1K $\Omega$	1
Resistor	1M $\Omega$	1
Capacitor	100nF	1
Capacitor	10nF	1
Jumper Wires		3

TABLE 0

### DESCRIPTION.

- 1) Giving power supply to Breadboard through connecting USB to micro USB board and give VCC(+5V) power supply and ground the respective rails in breadboard.
- 2) Generated clock using 555 timer by using two capacitors (10nF,100nF) , one resistor 1M $\Omega$  and jumper wires.It will the convert regular pulse into Square pulse.
- 3) Made a circuit using one Decoder(7447) used to covert binary input into specific output pattern, one X-OR gate(7486) and two D-Flip flops(7474) used to store a single bit of information.
- 4) Connected the Clock output of 555 timer circuit to Clock signal of D-Flip flops.
- 5) And make connections between the seven segment display and decoder. A seven segment display is a electronic display that can show numerical digits (0-9) and some additional characters.

### BLOCK DIAGRAM.

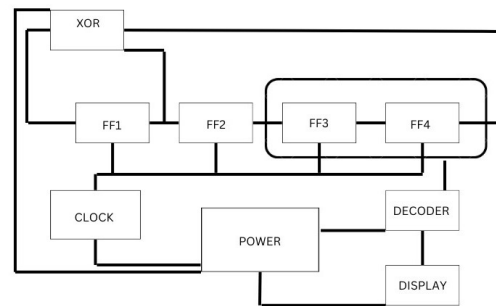


Fig. 5: Block Diagram

### Observation.

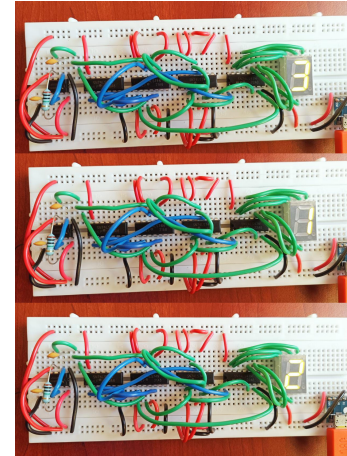


Fig. 5: OBSERVATIONS

Random Variables are observed in a A seven segment display, it is showing random numbers between (0-9) and some additional characters